

Name:
Honor Code:

K E Y

Realize

$$F(a,b,c,d,e) = \sum m(0, 1, 2, 19, 29, 30)$$

using a 16-1 MUX with the control inputs $a, b, c \& d$.

$$\begin{aligned} f &= a'b'c'd'e' + a'b'c'd'e + a'b'c'd'e' \\ &\quad + a'b'c'de + abcde' + abcde \\ &= a'b'c'd'(1) + a'b'c'd(e') + \\ &\quad a'b'c'd(e) + abcd'(e) + abcd(e') \\ &\quad + a'b'c'd'(0) + \dots (0) \end{aligned}$$

